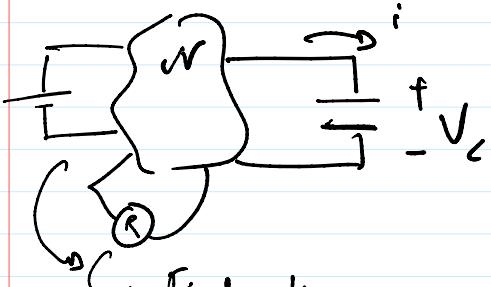


Fundamental Memory Elements

$$\begin{array}{c} \text{Q} = \frac{1}{C} V \\ -\frac{dQ}{dt} = C \frac{dV}{dt} \end{array}$$


$$Q = C V \quad \text{Capacitance}$$

$$i = \frac{dQ}{dt} = \frac{d(CV)}{dt} = C \frac{dV}{dt} \quad (\text{If } C \text{ is not a function of } V)$$



In Find time independent sources


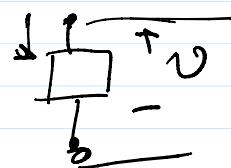
$V_C(t)$ is constant \therefore there are no time dependent sources
 $i = 0$



A capacitor with no voltage change can be modeled as

an open circ.


$$i = C \frac{dV}{dt}$$

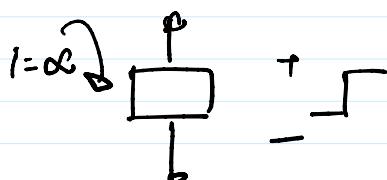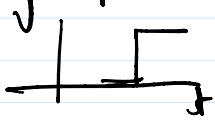

An abruptly changing voltage causes $\propto i$.

$\Rightarrow C$ can be modeled as a short under this condition.

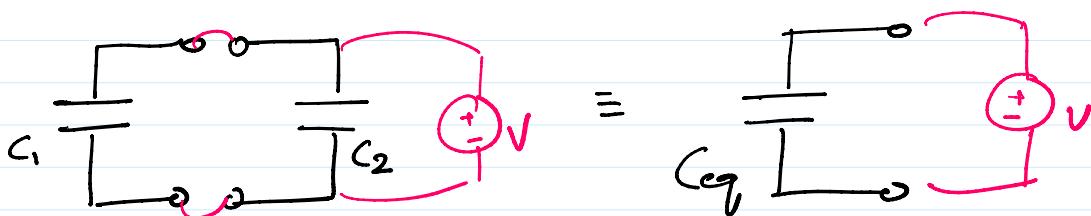
Equivalent Capacitance (Parallel / Series)



$$Q_{Total} = Q_1 V + Q_2 V \Leftrightarrow Q_{Total} = C_{eq} V$$

$$1/(parallel) = 1/Q_1 + 1/Q_2$$

$$C_{eq}(\text{parallel}) = C_1 + C_2$$

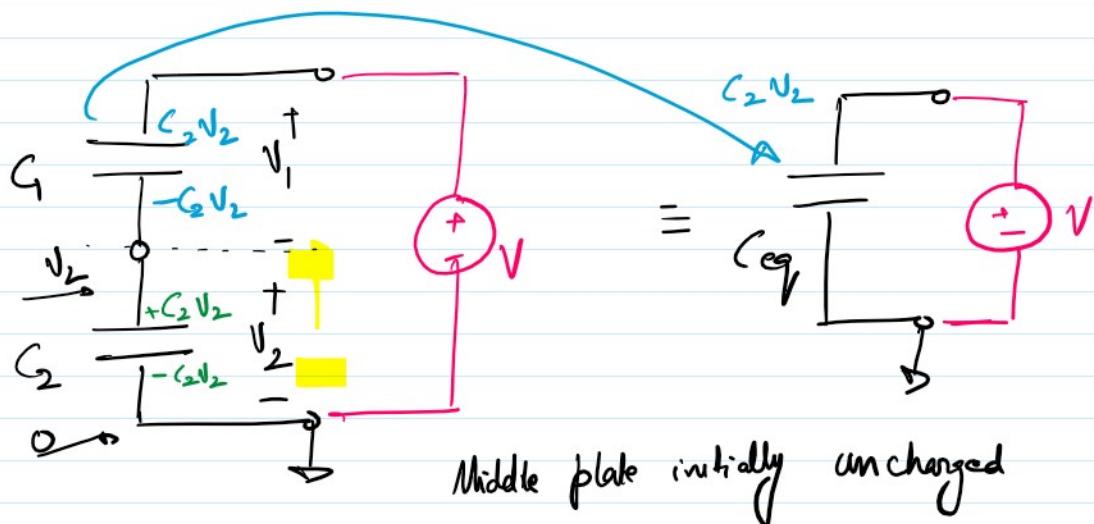

$$Q = C_2 V_2 \quad V_1 = \frac{Q}{C_1} = \frac{C_2 V_2}{C_1}$$

$$V = V_1 + V_2 = \left(\frac{C_2}{C_1} + 1 \right) V_2 = \frac{C_1 + C_2}{C_1} V_2$$

$$\Rightarrow V = \left(\frac{C_1 + C_2}{C_1 C_2} \right) Q$$

$$C_{eq}(\text{series}) = \frac{C_1 C_2}{C_1 + C_2}$$

Charge conservation (in isolated systems)
in capacitors.


$$C_1 \frac{V_1}{C_1} - V_1 \quad C_2 \frac{V_2}{C_2} - V_2 \quad \frac{V}{C_1} - \frac{V}{C_2}$$

$$Q_{\text{Total}} = C_1 V_1 + C_2 V_2 \quad Q_{\text{Total}} = C_{eq} \cdot V$$

$$\Rightarrow V = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2} \quad = (C_1 + C_2) V$$




TRANSIENT

ANALYSIS

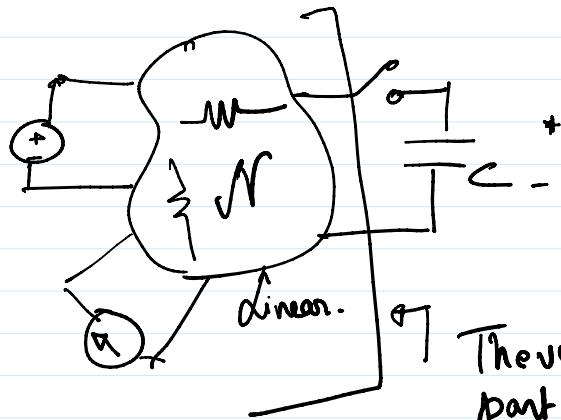

Assume C is initially unchanged.



Thevenize the non-Capacitive part.

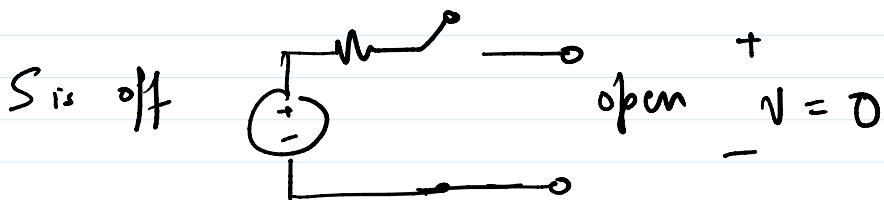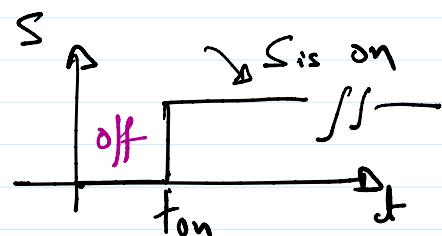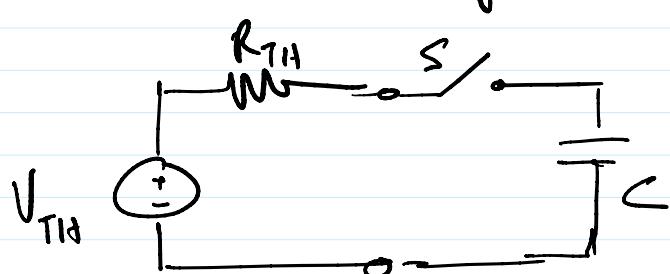


at $t = 0$

$$V_C = V_{TH}$$

$$\text{at } t = t_{on}$$

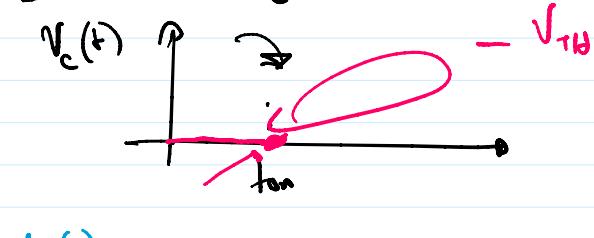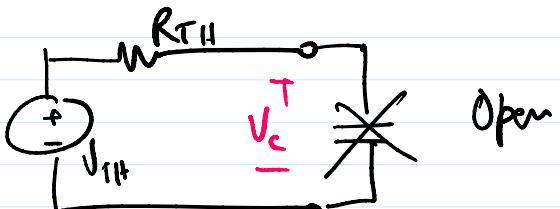
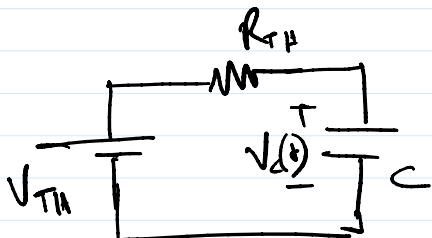
$$V_C(t) = \begin{cases} V_{TH} & t < t_{on} \\ -V_{TH} & t \geq t_{on} \end{cases}$$




$$\frac{V_{TH} - V_C(t)}{R_{TH}} = C \frac{dV_C}{dt}$$

$$\Rightarrow \frac{dV_C}{dt} + \frac{1}{R_{TH}C} V_C(t) = \frac{V_{TH}}{R_{TH}}$$

$$V_C(t) = V_{TH} \left(1 - e^{-t/(R_{TH}C)} \right)$$
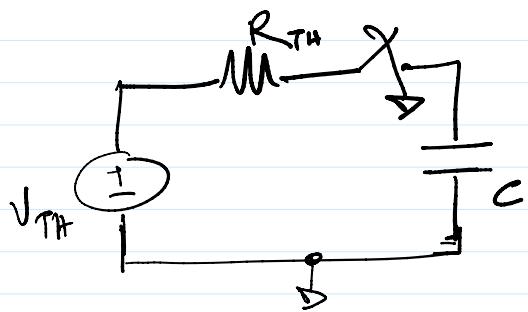
$$V_C(t) = V_{TH} \left(1 - e^{-t/R_{TH}C} \right)$$





C has an initial charge.

of $Q(0)$.

$$V_C(0) = \frac{Q(0)}{C}$$

$$V_C(t) = V_C(0) + (V_{final} - V_C(0)) \left(1 - e^{-t/R_{TH}C} \right)$$



$$R_{TH}C = \text{Time constant}$$

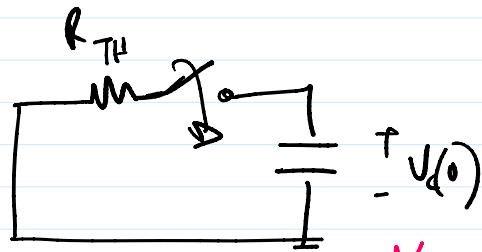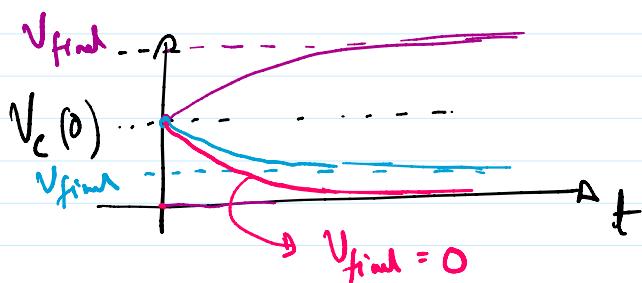


$$V_C(t) = V_C(0) e^{-t/R_{TH}C}$$



Natural Response of the ckt.

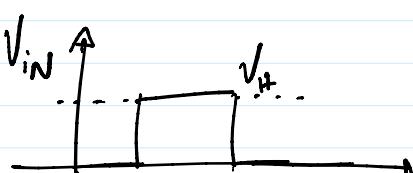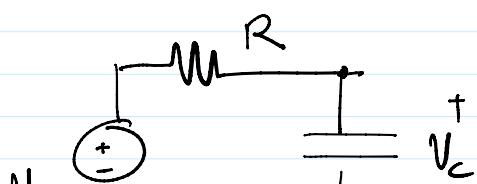Natural Response: Response to initial condition.






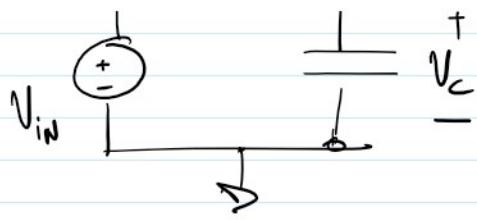


Initially C is uncharged.

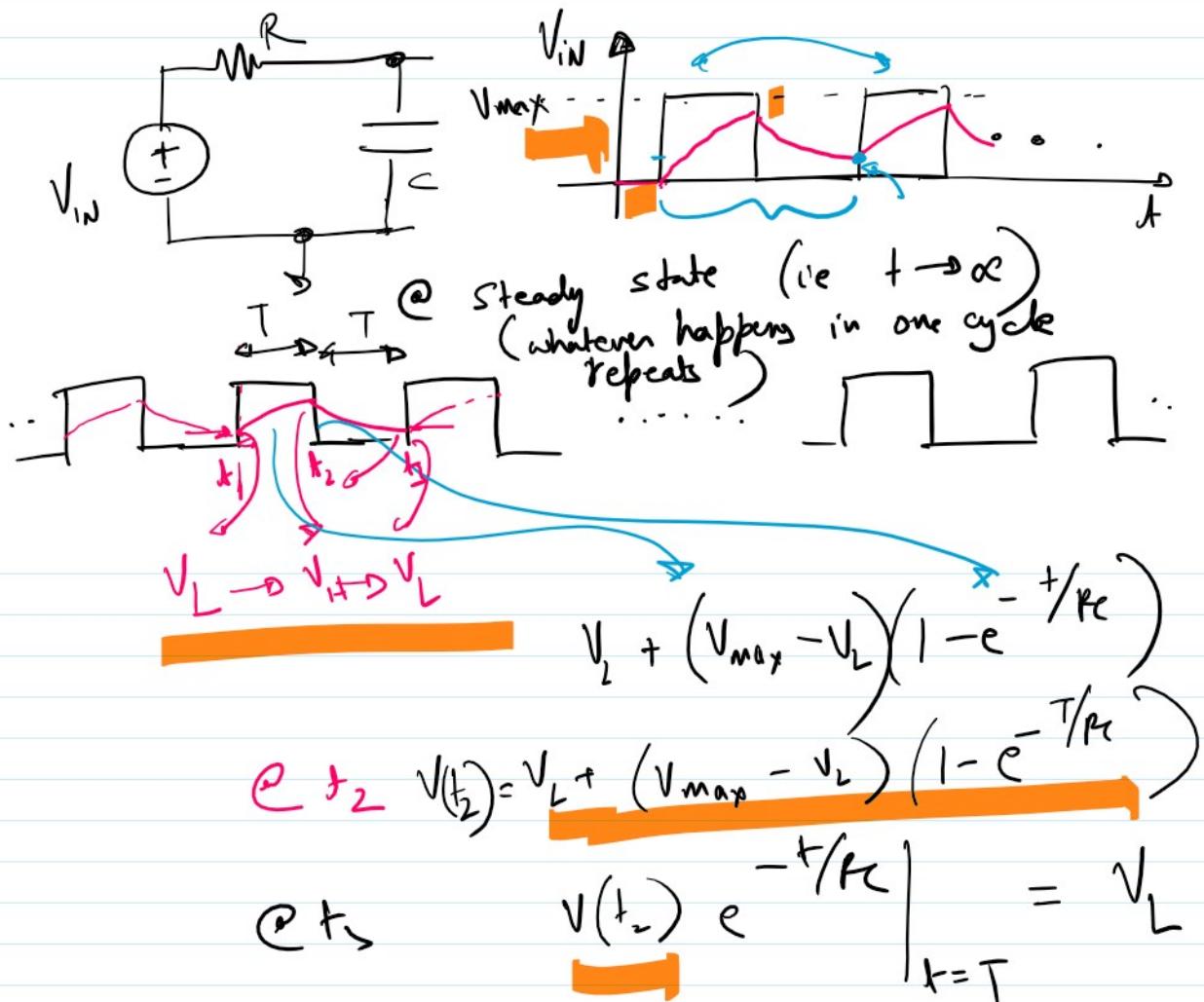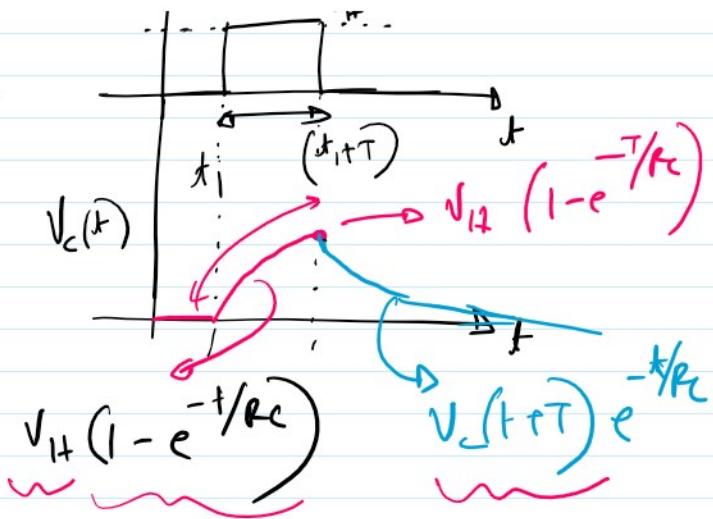

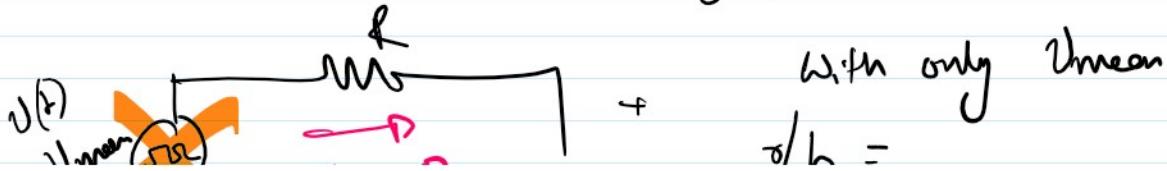
$$N(t) = \overline{V}_{mean} + \underbrace{(V(t) - \overline{V}(t))}_{\text{O mean}}$$



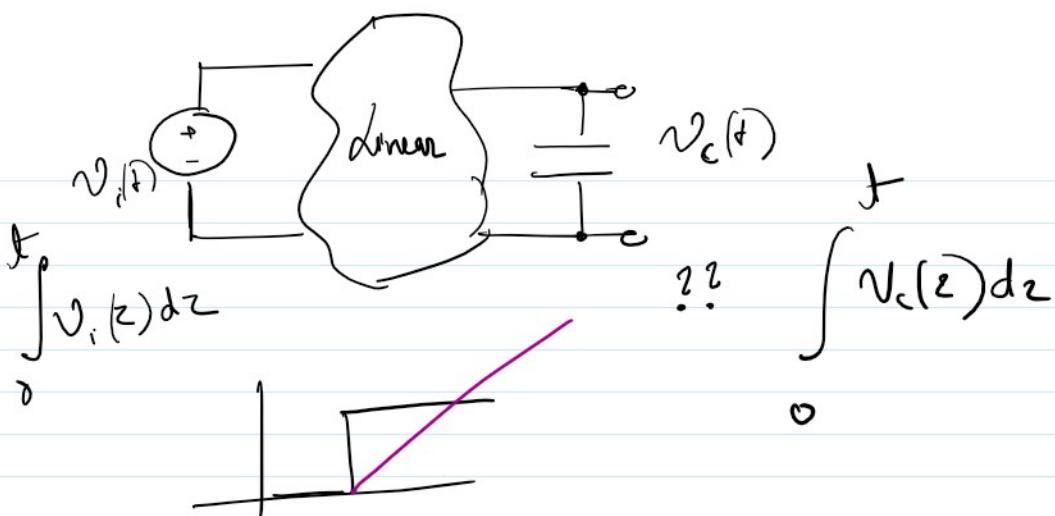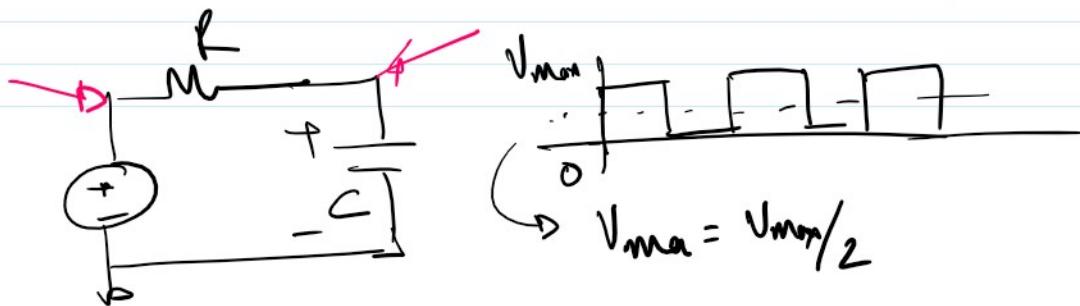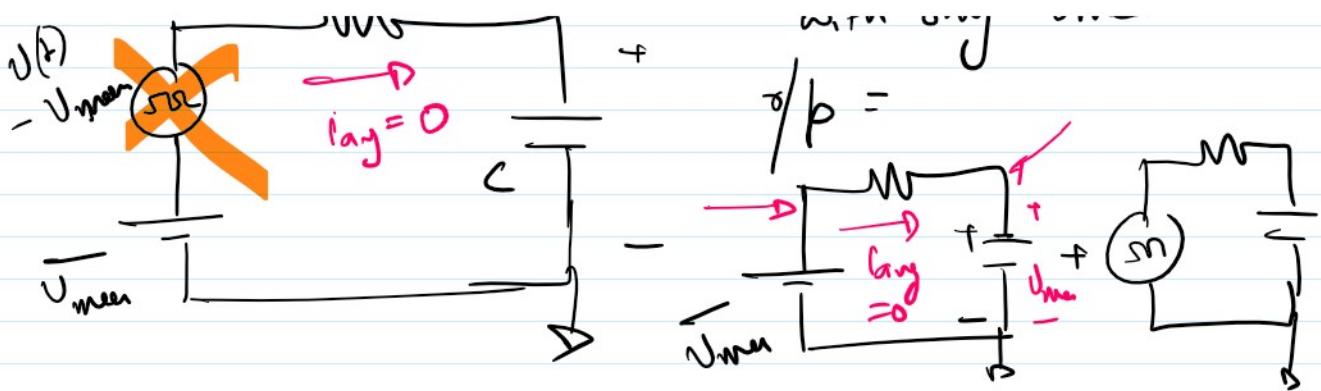

Time-variant Steady State Response

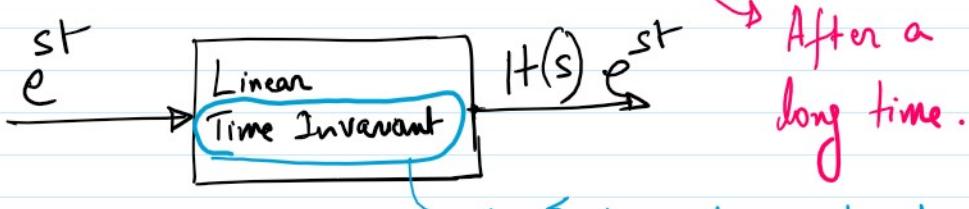

Time Invariant

away from



System does not change with time,
e.g.: No switching inside.

$$e^{j\omega t} = \cos(\omega t) + j \sin(\omega t)$$

$$\begin{aligned}\cos(\omega t) &= \frac{1}{2} [e^{j\omega t} + e^{-j\omega t}] \\ \sin(\omega t) &= \frac{1}{2j} [e^{j\omega t} - e^{-j\omega t}]\end{aligned}$$

Can be applied
through signal
gen.

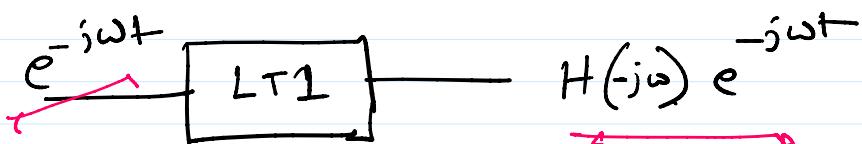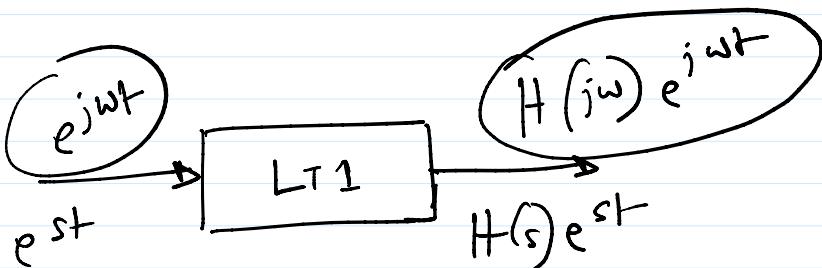Cannot be applied through sig. gen
BUT convenient for analysis.




$$H(j\omega) = |H(j\omega)| e^{j\phi(\omega)}$$

$$\dots \nearrow \quad \swarrow \quad \nearrow \quad \searrow$$

$$|H(j\omega)| \quad \phi(\omega) \quad |H(-j\omega)| \quad \phi(-\omega)$$

$$H(j\omega) = |H(j\omega)| e^{j\phi(-\omega)}$$

$$H(-j\omega) = |H(-j\omega)| e^{-j\phi(-\omega)}$$

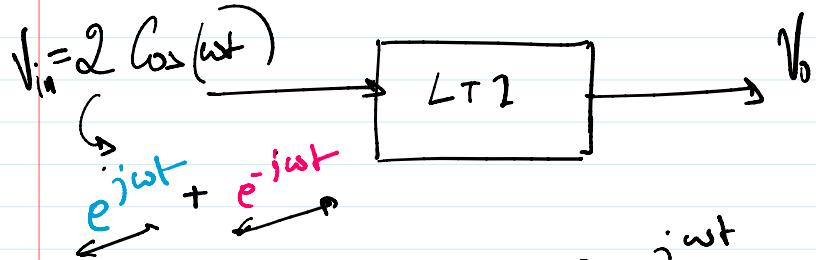

$$V_o = H(j\omega) e^{j\omega t} + H(-j\omega) e^{-j\omega t}$$



$$= |H(j\omega)| e^{j(\omega t + \phi(\omega))} + H(-j\omega) e^{-j(\omega t + \phi(-\omega))}$$

$$V_o(t) = |H(j\omega)| \cos(\omega t + \phi(\omega)) + i |H(j\omega)| \sin(\omega t + \phi(\omega))$$


$$+ |H(-j\omega)| \cos(\omega t - \phi(-\omega)) - i |H(-j\omega)| \sin(\omega t - \phi(-\omega))$$

~~r^0~~

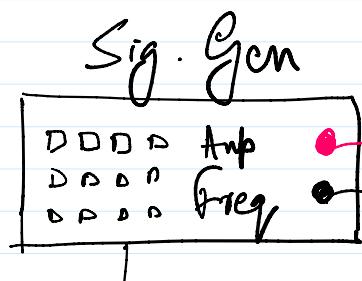
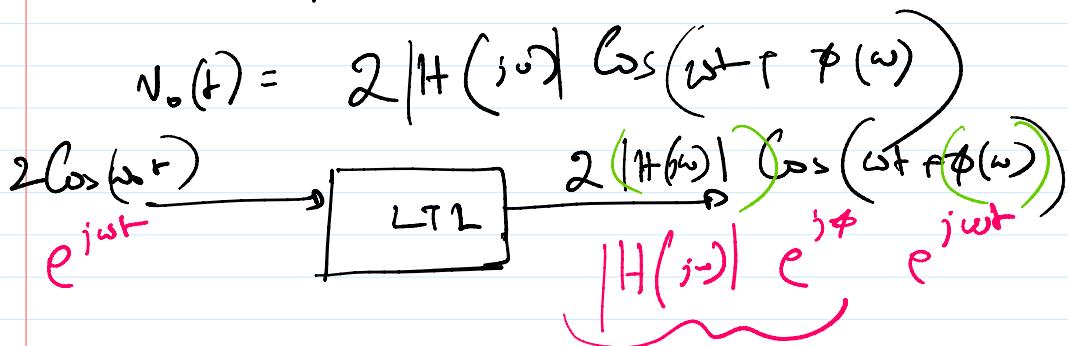
$$\left. \begin{array}{l} H(j\omega) = H(-j\omega) \\ \phi(\omega) = -\phi(-\omega) \end{array} \right\} \text{Real Systems}$$





Signal

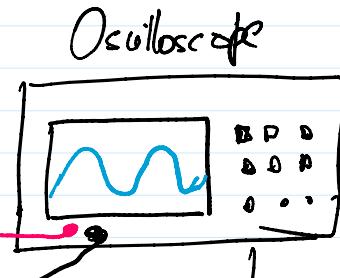

Amp

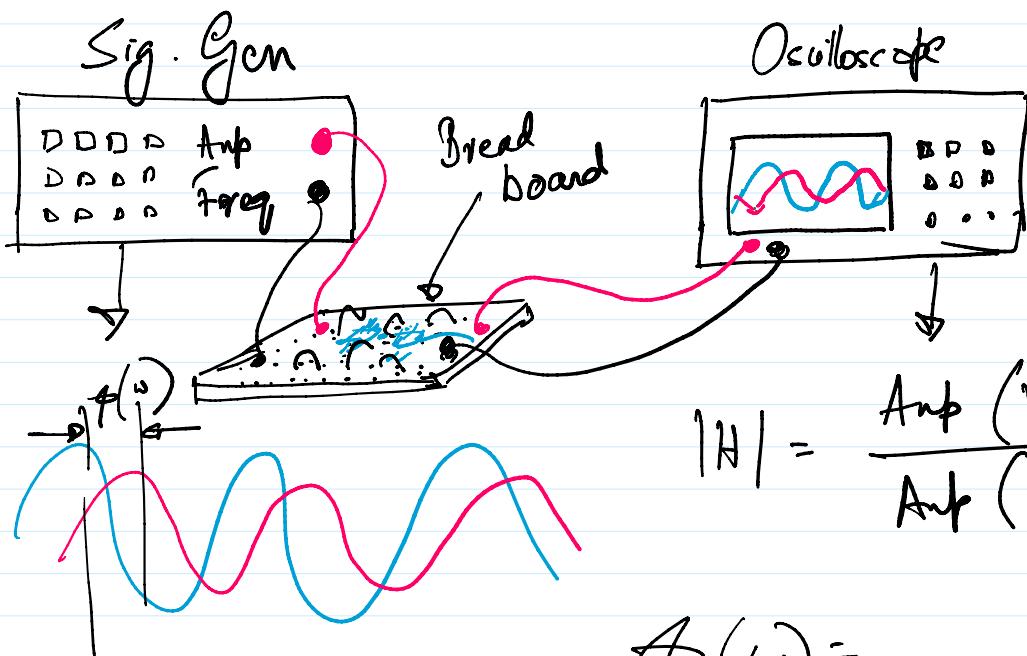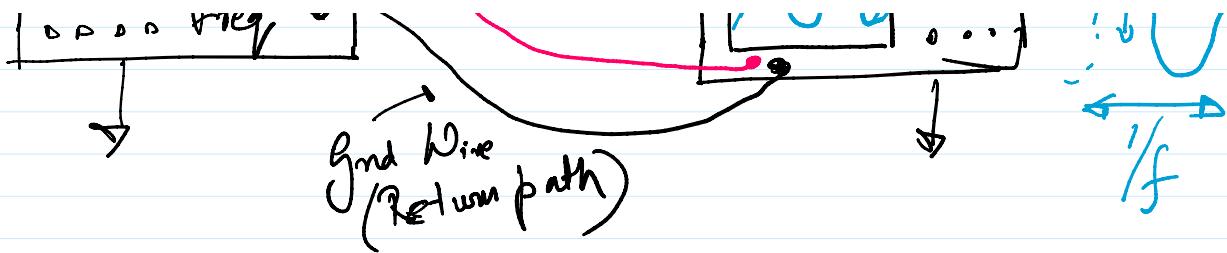

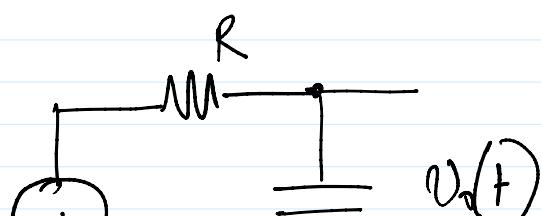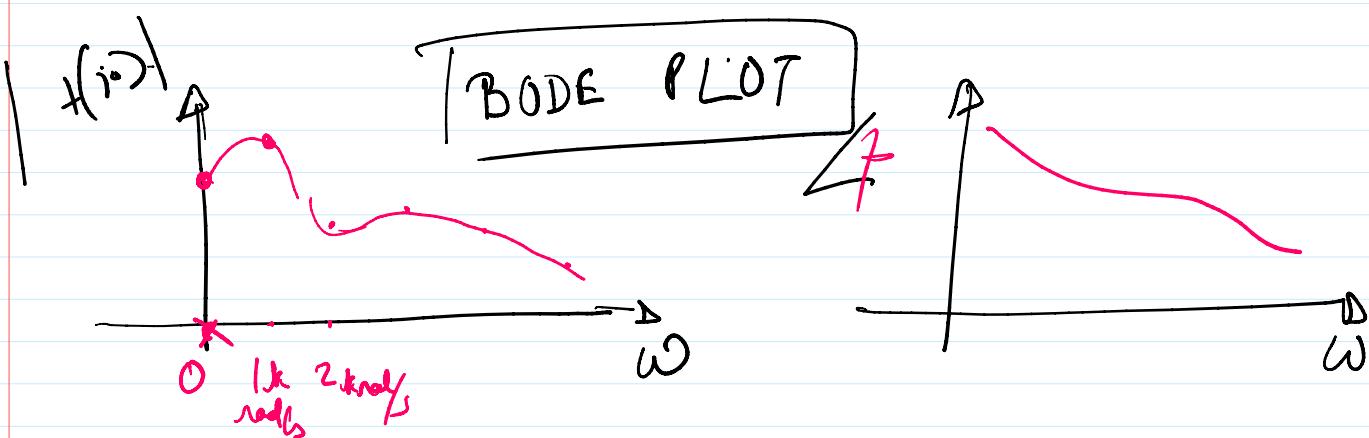$\phi(\omega) =$
 $H(j\omega) = \text{Transfer Function (TF)}$



$$\frac{dV_o}{dt} + \frac{V_o}{L} = \frac{V_i}{C}$$


$$\frac{1}{jC} V_i(t) = H(s) e^{st}$$

$$s H(s) e^{st} + \frac{1}{RC} H(s) e^{st} = \frac{e^{st}}{RC}$$

$$\Rightarrow H(s) = \frac{1}{1 + sRC}$$

$$H(j\omega) = \frac{1}{1 + j\omega RC}$$
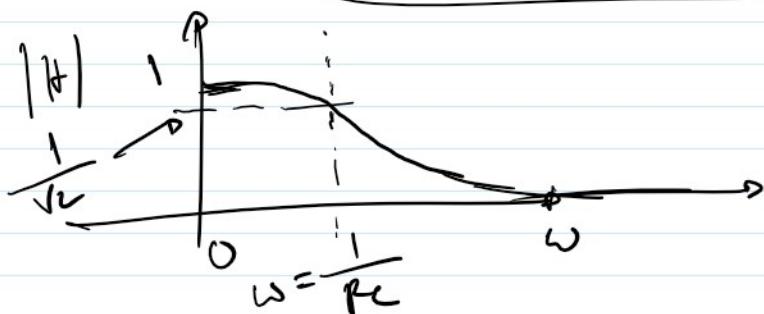
$$H(j\omega) = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$



Impedance of a Capacitor

$$i(t) = C \frac{dV}{dt} = sC e^{st}$$

$$V_i = e^{st}$$

$$Z(s) = \frac{V_C(s)}{I_C(s)} = \frac{1}{sC}$$

$$Z(j\omega) = \frac{V_C(j\omega)}{I_C(j\omega)} = \frac{1}{sC}$$

$$Z(j\omega) = \frac{1}{j\omega C}$$

$$\boxed{Z(j\omega) = \frac{1}{j\omega C}}$$

L

